

ELEC-E4440 - Microwave Engineering Workshop



*A 1.5 GHz Doppler Radar*

SIHAN SHAO  
YIFAN YU
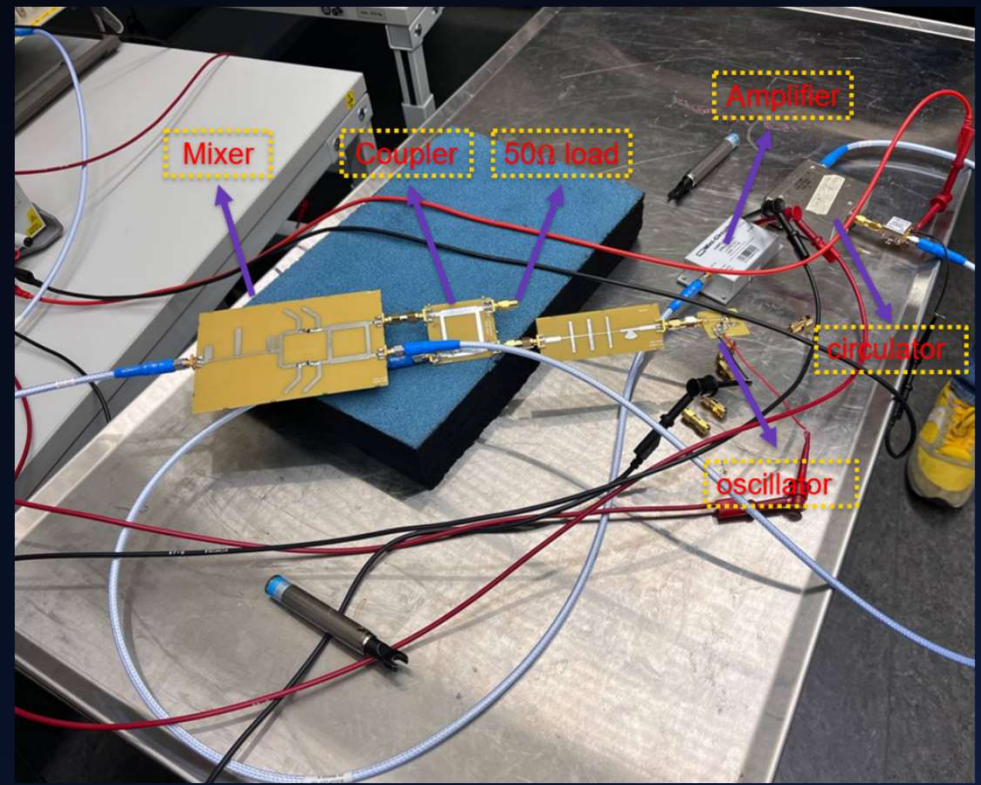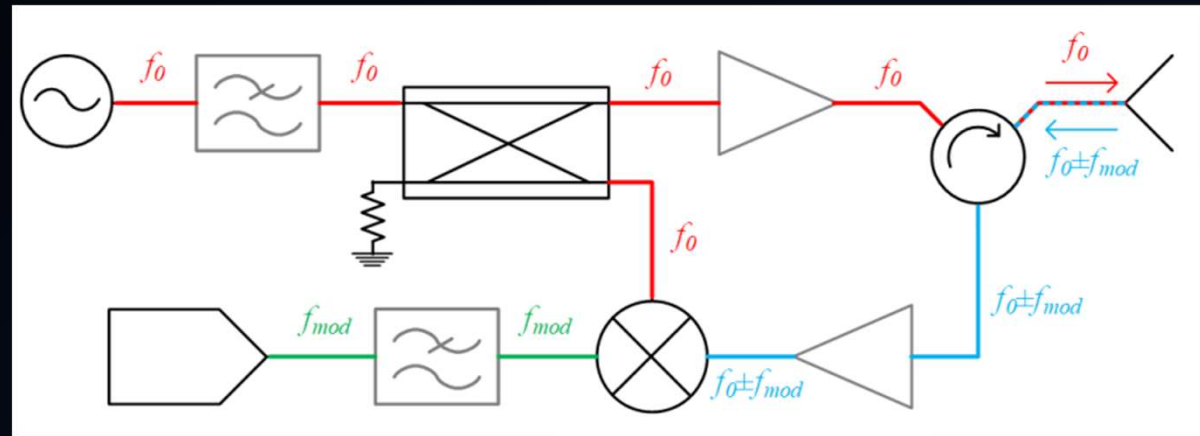
## Work Division

- Sihan: LPFs, Coupler, Mixer
- Yifan: Oscillator, Amplifier

Our presentation will roughly follow the order in which the signal flows



# Results


Calculated	Measured
1.75m	1.32m

- Oscillator output power: 5 dBm
- Cable insertion loss: 1 dB (estimate)
- LPF insertion loss: 0.69 dB
- PA gain: 24 dB
- Coupler insertion loss: 3.6 dB
- Circulator insertion loss: 0.5 dB
- Total transmitted power: 23.21 dBm (209 mW)

$$\left( \frac{P_t G G \sigma \lambda^2}{(4 \pi)^3 S_{min}} \right)^{1/4}$$



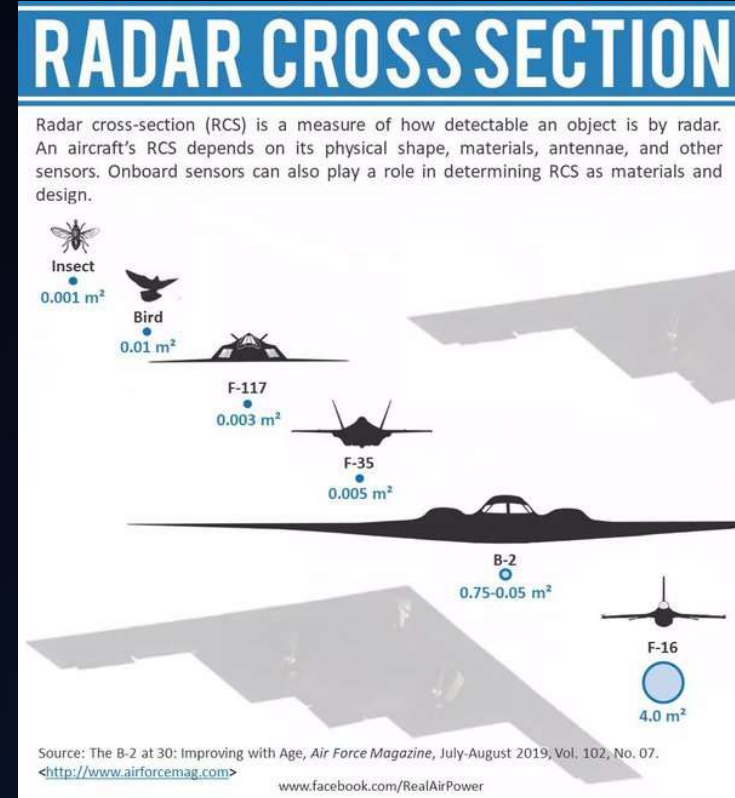
1.74733

- Antenna Gain: 9 dBi (7.94)
- Radar cross section: 0.035 m<sup>2</sup>
- Wavelength: 0.2 m
- Noise floor: -60 dBm (S<sub>min</sub> = 1 uW)


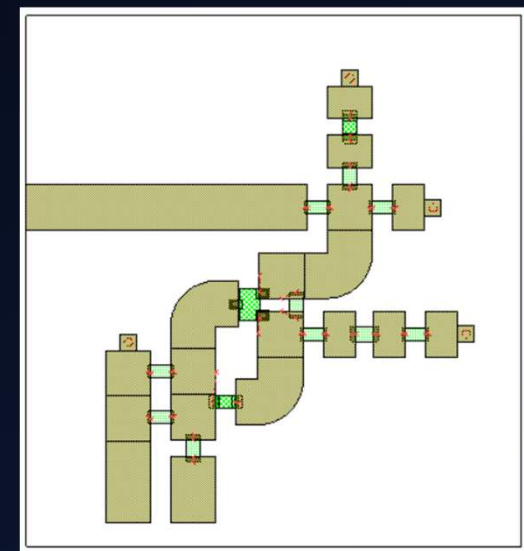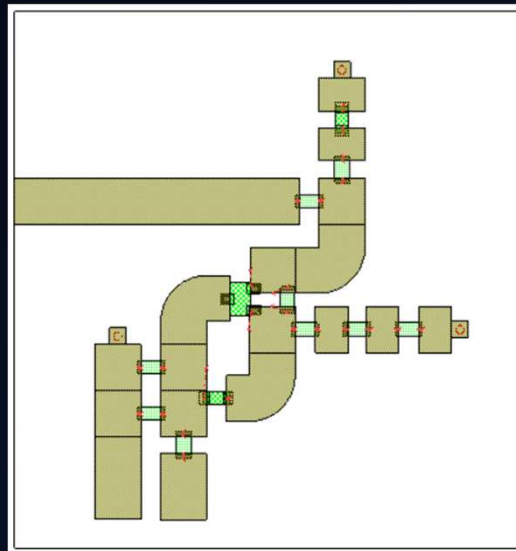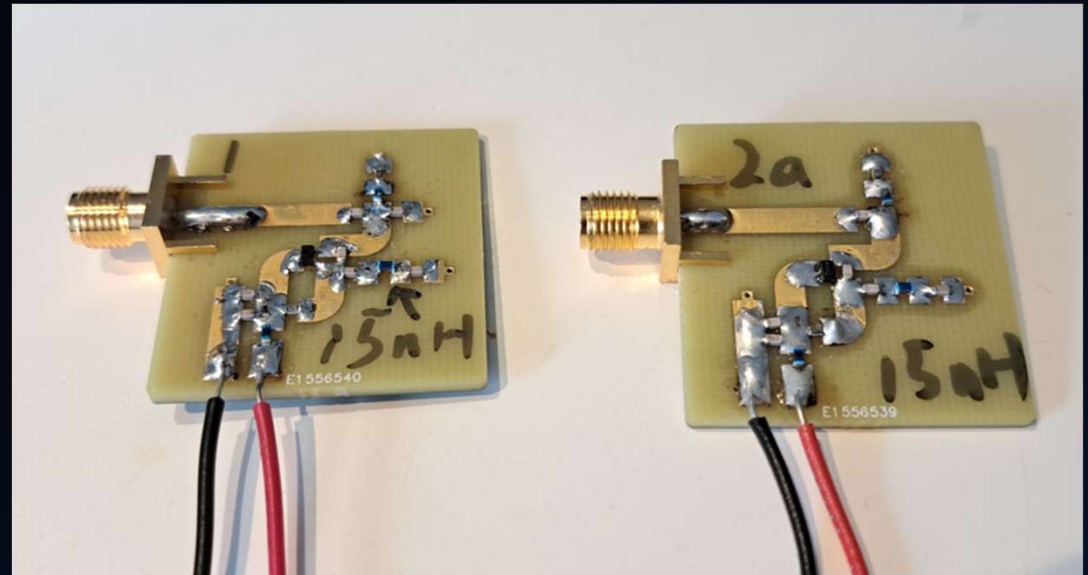
# Oscillator (two versions)


- Left: Version 1, Original Clapp oscillator
- Right: Version 2, “Degenerated Clapp” achieving higher output power






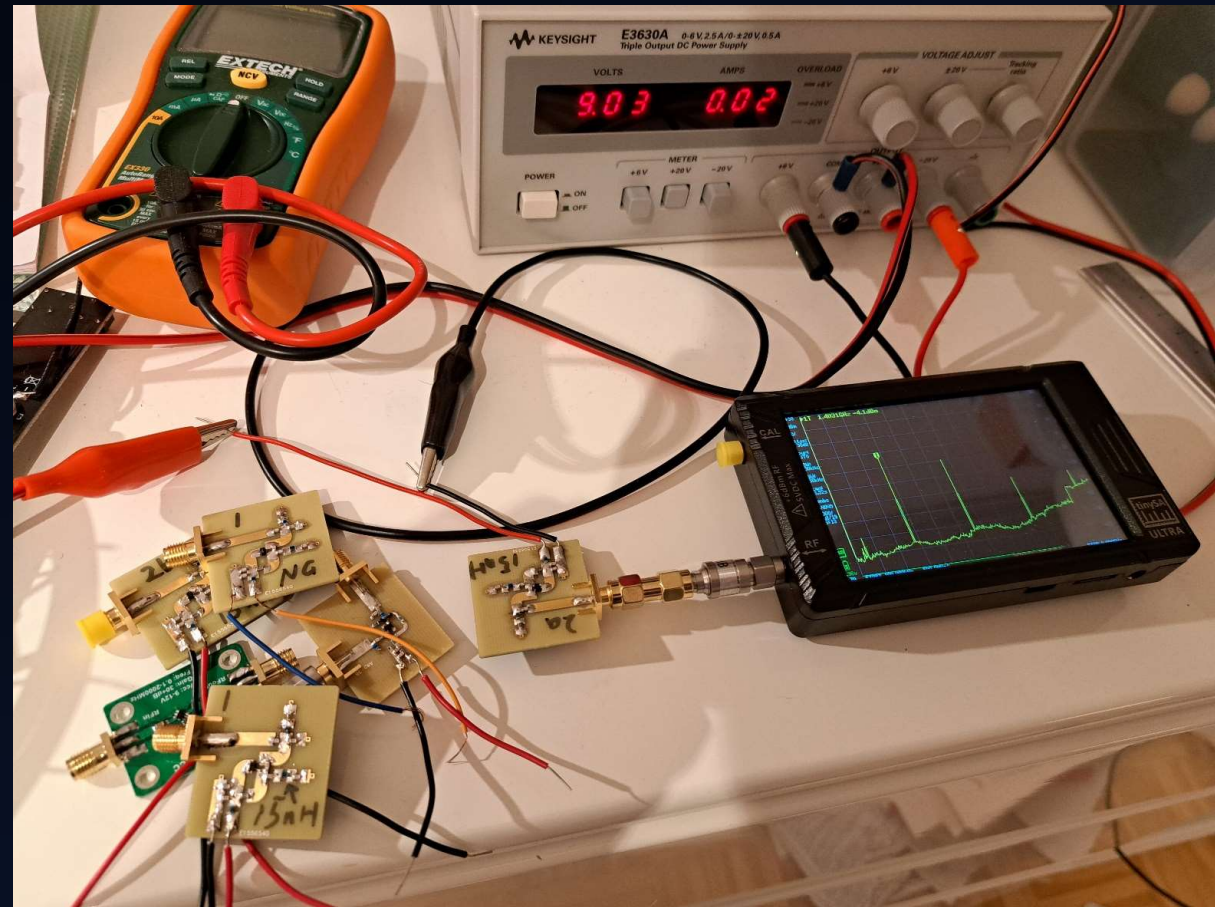
# Measurement Setup

- Supply voltage: 9V
- tinySA Ultra: 0 to 6 GHz
- External 10 dB attenuator (tinySA input max. 6 dBm)




# Measurement Setup (Version 2 only)

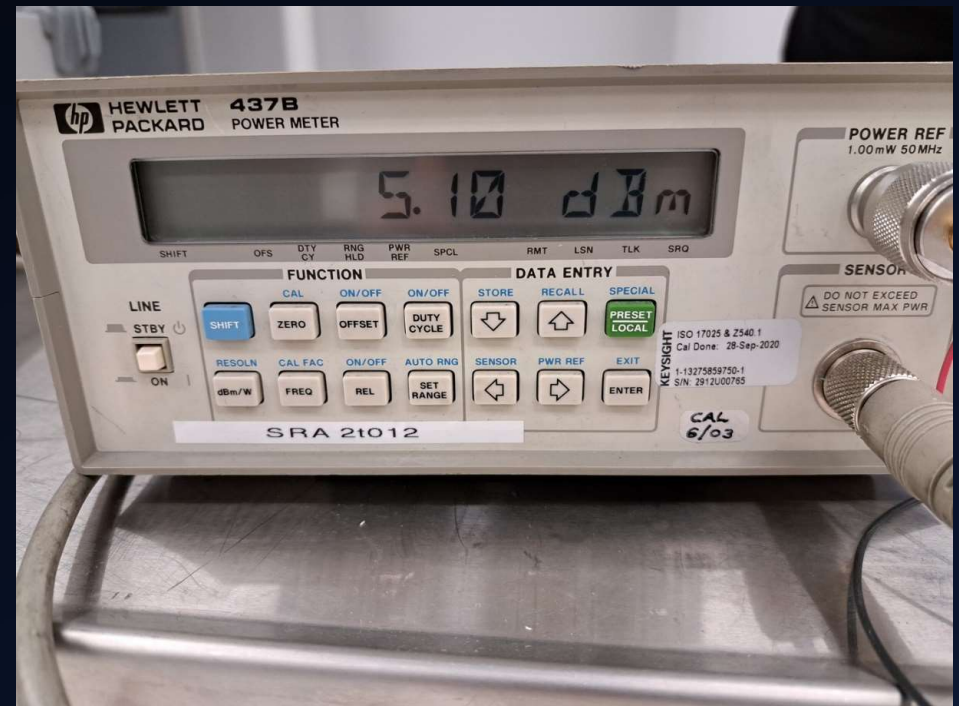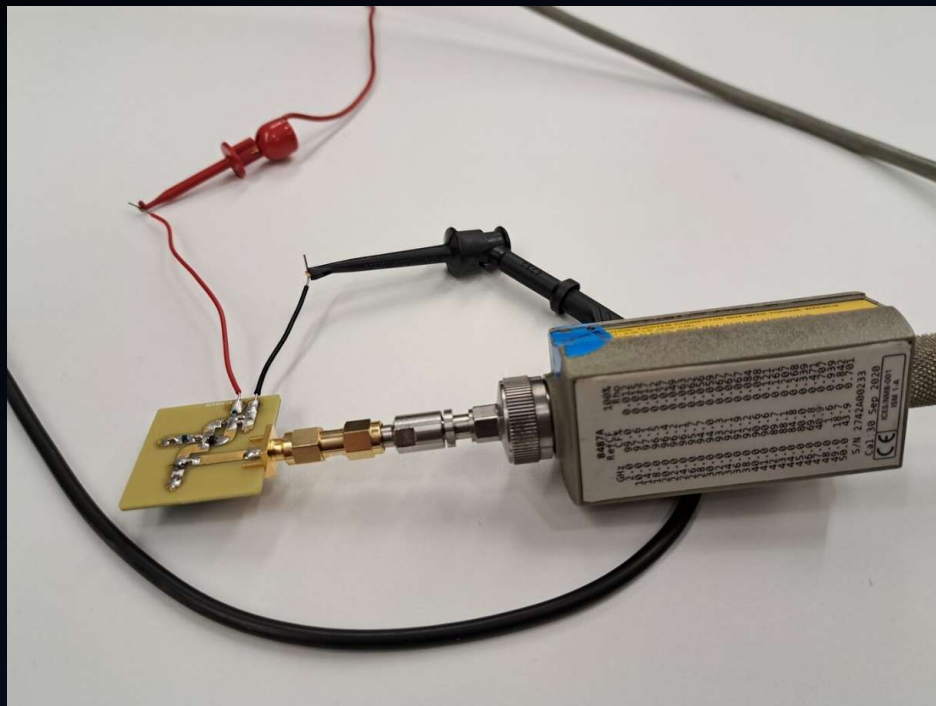


Measured Total Output Power: 5.1 dBm


# Output Power: Original Clapp

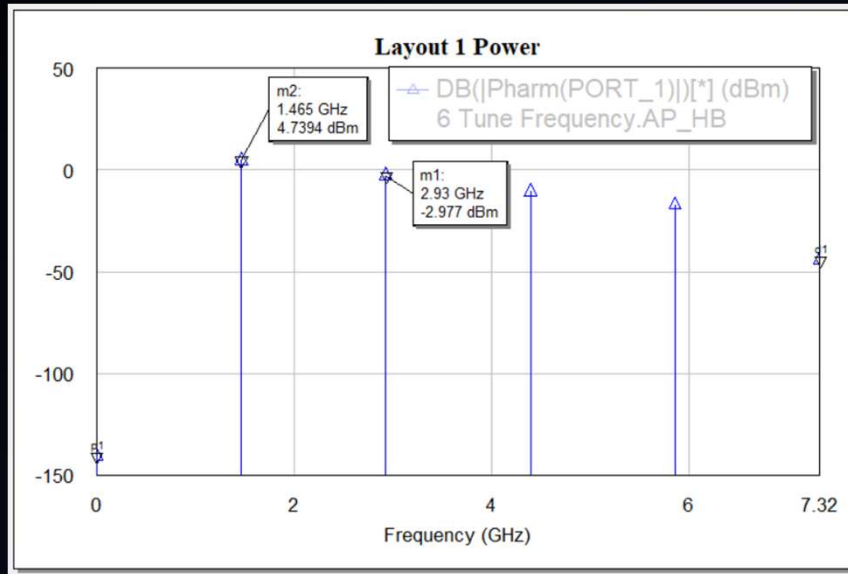

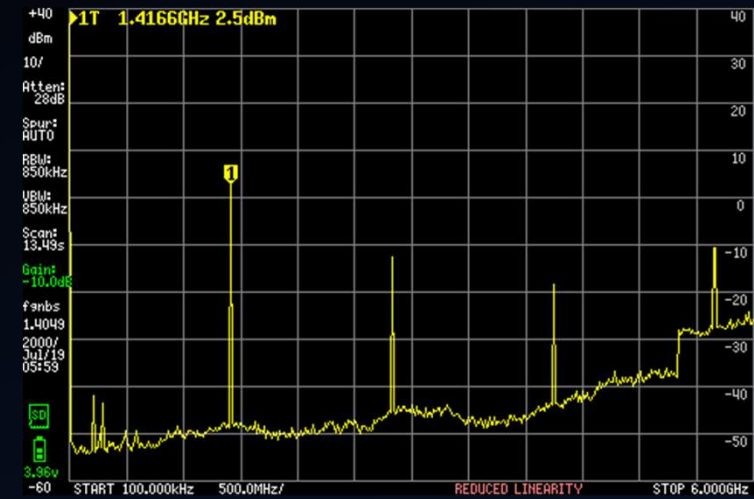
- Simulated Output Power: 4.7 dBm at 1.47 GHz
- Measured Output Power: 1.4 dBm at 1.42 GHz




Power reduces as the transistor heats up

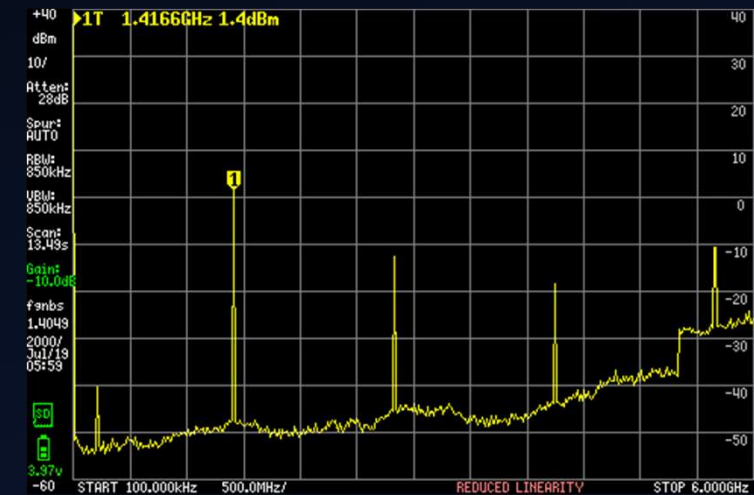

# Output Power: Improved Design

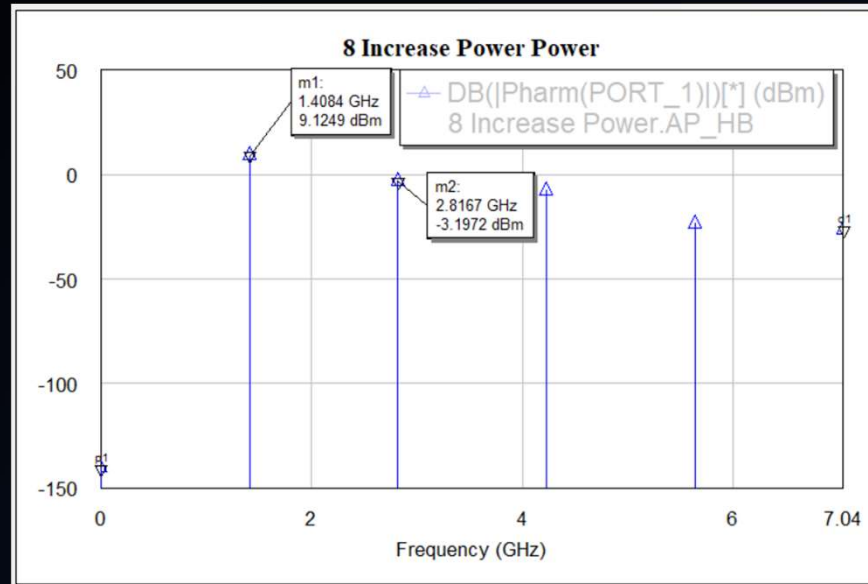

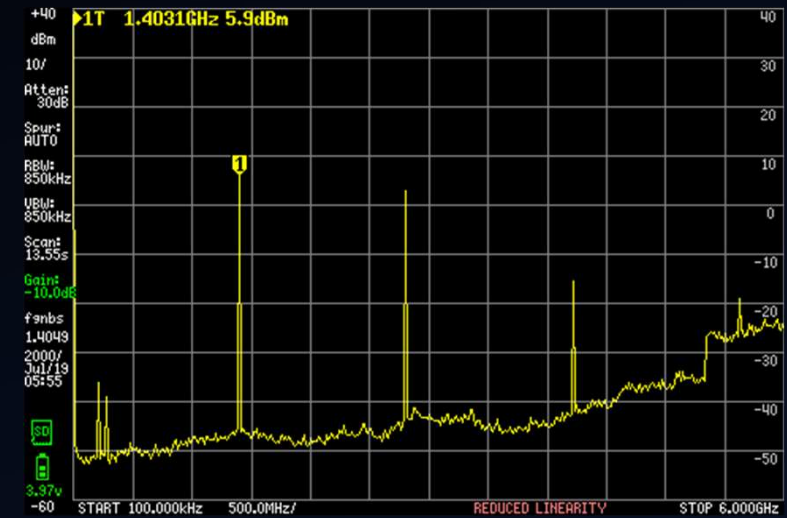- Simulated Output Power: 9.1 dBm at 1.41 GHz
- Measured Output Power: 5.3 dBm at 1.4 GHz



Power reduces as the transistor heats up





# Filter Design

## LOW-PASS FILTER AFTER OSCILLATOR


- The oscillator generates a signal at around 1.5GHz
- Harmonic signals such as 3GHz and 4.5 GHz should be eliminated

## LOW-PASS FILTER AFTER MIXER


- The mixing process generates various frequencies, and the desired frequency is about a few MHz
- Harmonic signals such as 1,5 GHz to 6 GHz should be eliminated

# Filter Design

LOW-PASS FILTER AFTER OSCILLATOR

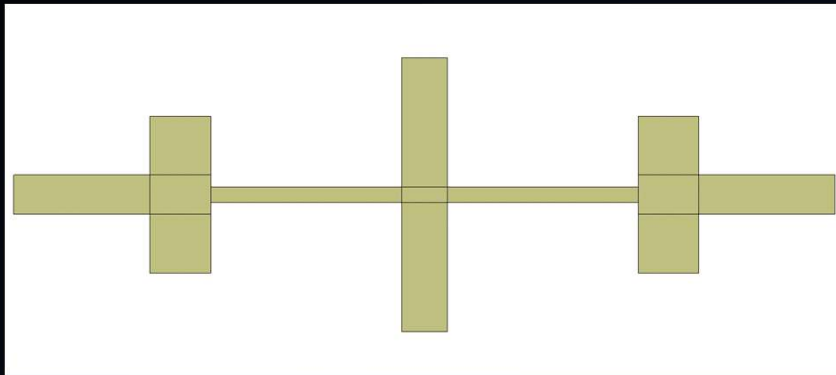


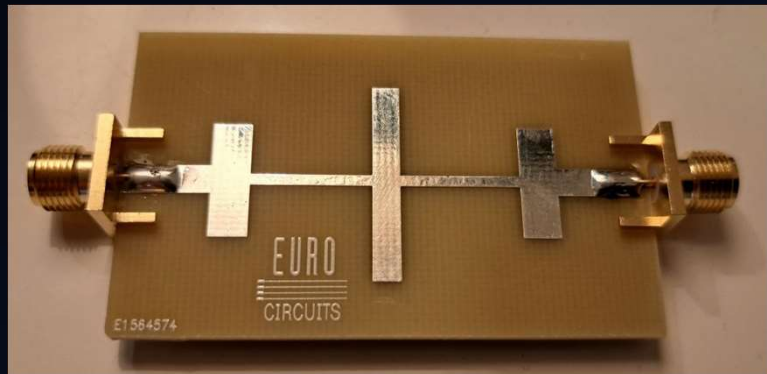a) Layout 1<sup>st</sup> of Low-pass filter on AWR




c) Prototypes of Manufactured LPF

LOW-PASS FILTER AFTER MIXER

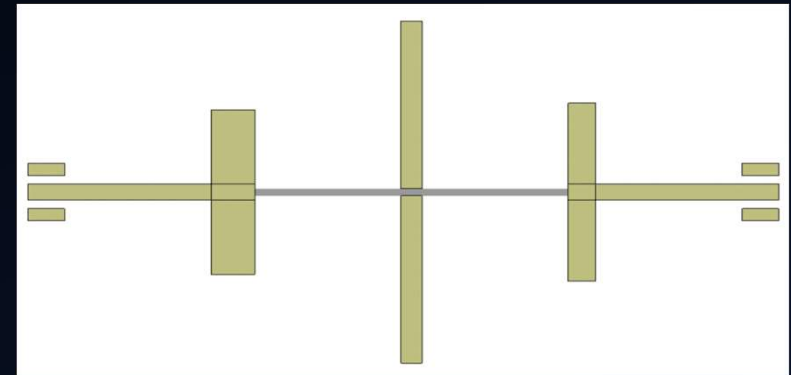

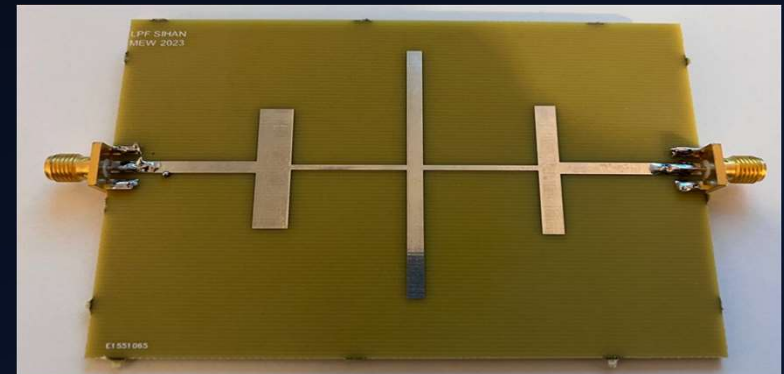b) Layout of 2<sup>nd</sup> Low-pass filter on AWR






d) Prototypes of Manufactured LPF

# Filter results
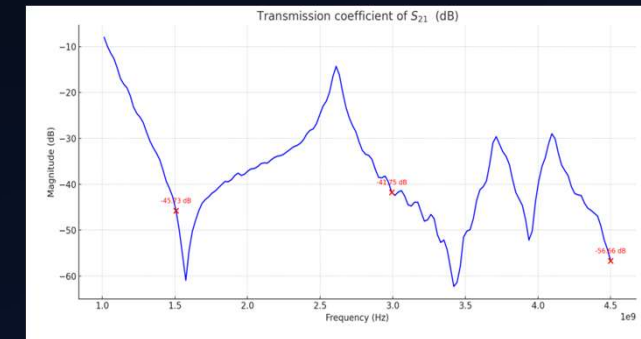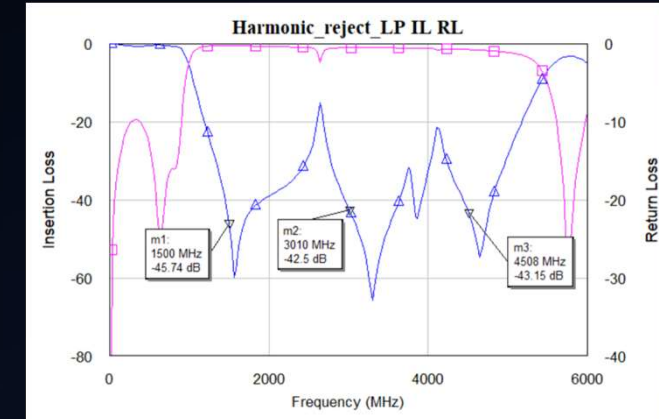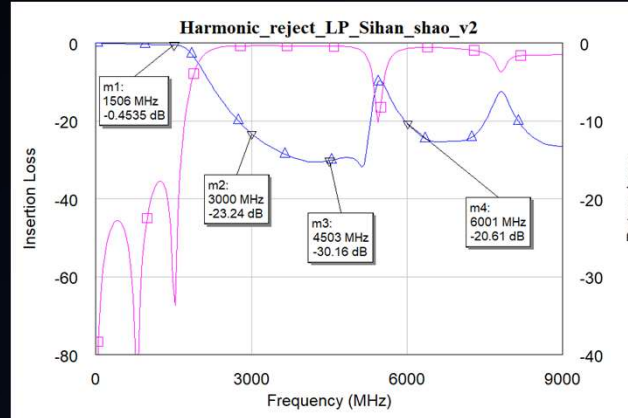
## HARMONIC REJECT FILTERS

- Effectively targets specific frequency points
- Removes undesired frequency components



a) Low-pass filter after oscillator

b) Low-pass filter after mixer




# Hybrid Coupler

- **FUNCTION**


- Splits or combines signals while maintaining phase relationship

- **PERFORMANCE**

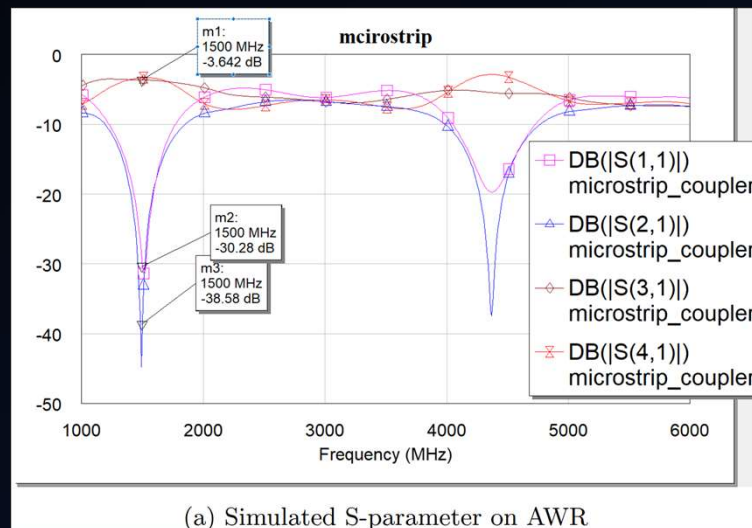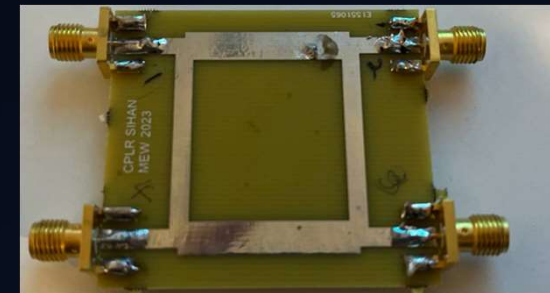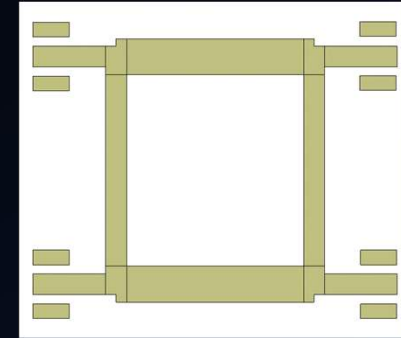- Transmission coefficients ( $S_{21}$ ,  $S_{31}$ ) close to simulated values (-4.92dB, 5.37dB vs. -3.642dB)
- Power distribution is nearly equal, showing strong performance




(a) Simulated S-parameter on AWR

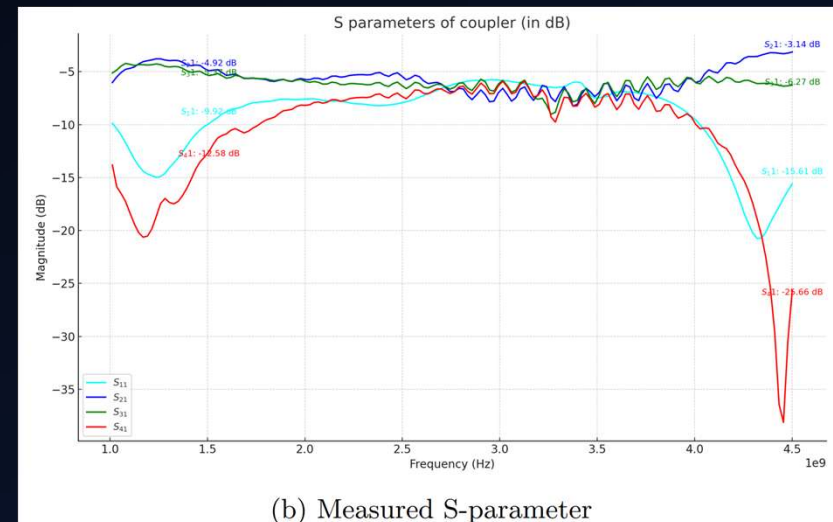


(b) Measured S-parameter
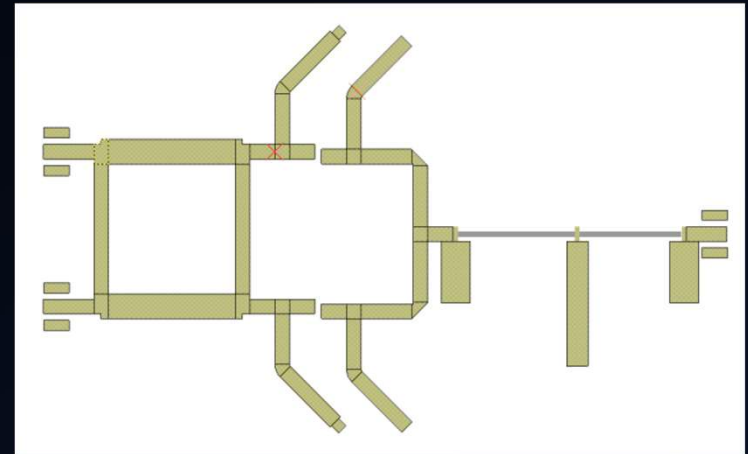
# Mixer Design

- **DESIGN CONSIDERATIONS**
  - Ground-end microstrip lines as inductors, accounting for parasitic effects and limited choices
  - Open-ended microstrip lines as capacitors for impedance control
  - Microstrip lines introduces less lossy comparing with lumped elements
- **OUTPUT HANDLING**
  - Mixer produces various frequency products
  - Design of a specialized low-pass filter to reject RF, LO, and harmonic signals simultaneously




a) Layout of Mixer on AWR

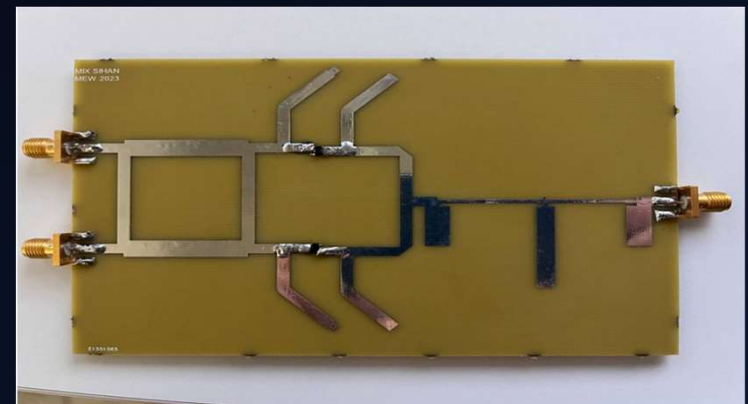


b) Prototypes of Manufactured Mixer



# Mixer Results

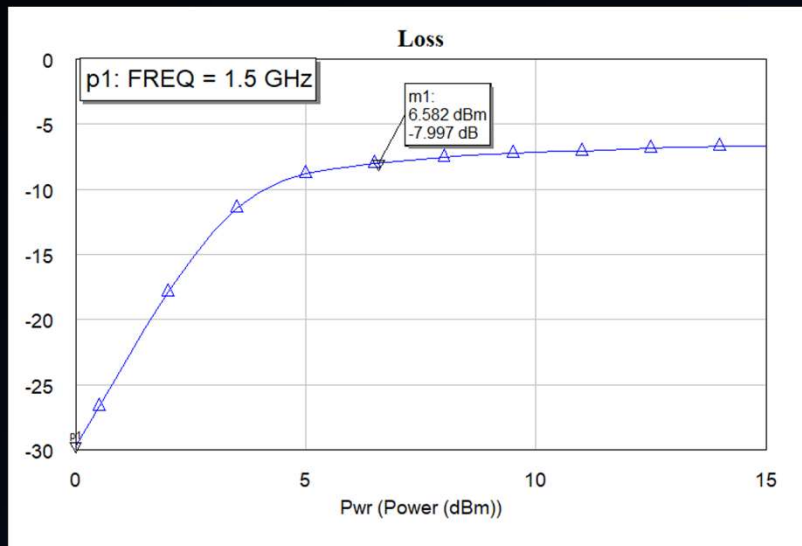

a) Simulated Conversion Loss on AWR

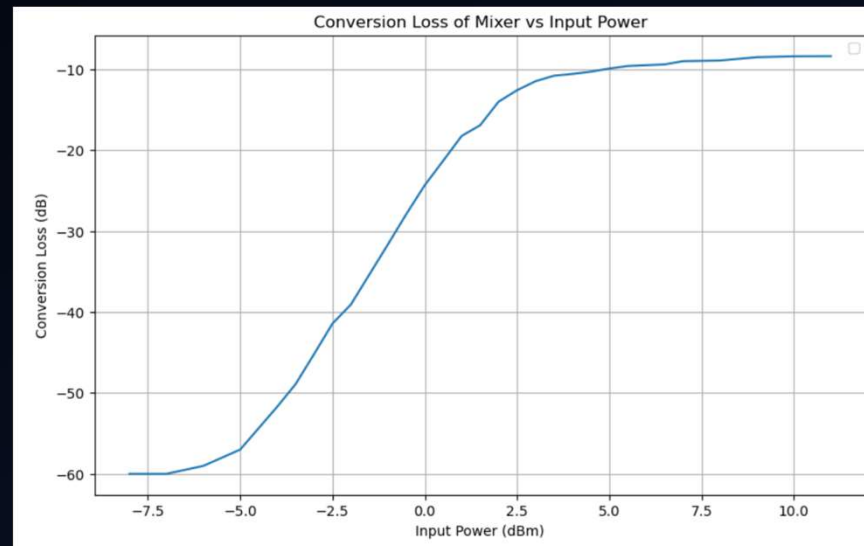

b) Measured Conversion Loss

Comparing the practical and simulated results between 0dB and 15dB, we observe a very similar overall trend, which indicates the good performance of our mixer.


# Problems and Future Optimizations

## 1. Optimization of Oscillator:

- Output power instability
- Frequency sensitivity
- Harmonics reduction
- Use transmission lines instead of discrete LC components to construct the resonant circuit
- Use temperature-compensated bias network
- Add shielding?



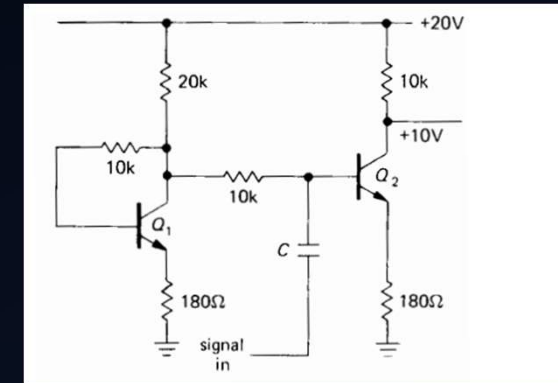a) hot air significantly decreases the output power



b) one possible temperature-compensated bias network

## 2. Optimization of passive components:

- miniaturization of components can reduce the lossy of our system



**Thanks for your Attention !**